

- Q.1 What do you understand by magnetic flux?
- Q.2 What is the meaning of electro-magnetic induction?
- Q.3 Write the Faraday's law's of electro-magnetic induction. (Faraday's)

Ans. 1 Magnetic Flux:- The total no. of magnetic lines of force normally passing through the unit cross section area of the magnetic field is called magnetic flux, represented by ϕ or ϕ_m .


where, $A \rightarrow$ cross section Area

$$\phi = \vec{B} \cdot \vec{A}$$

$B \rightarrow$ Magnetic field. $\phi = BA \cos\theta$

SI unit:- Weber (Wb)

C.G.S. Unit:- Maxwell (max)

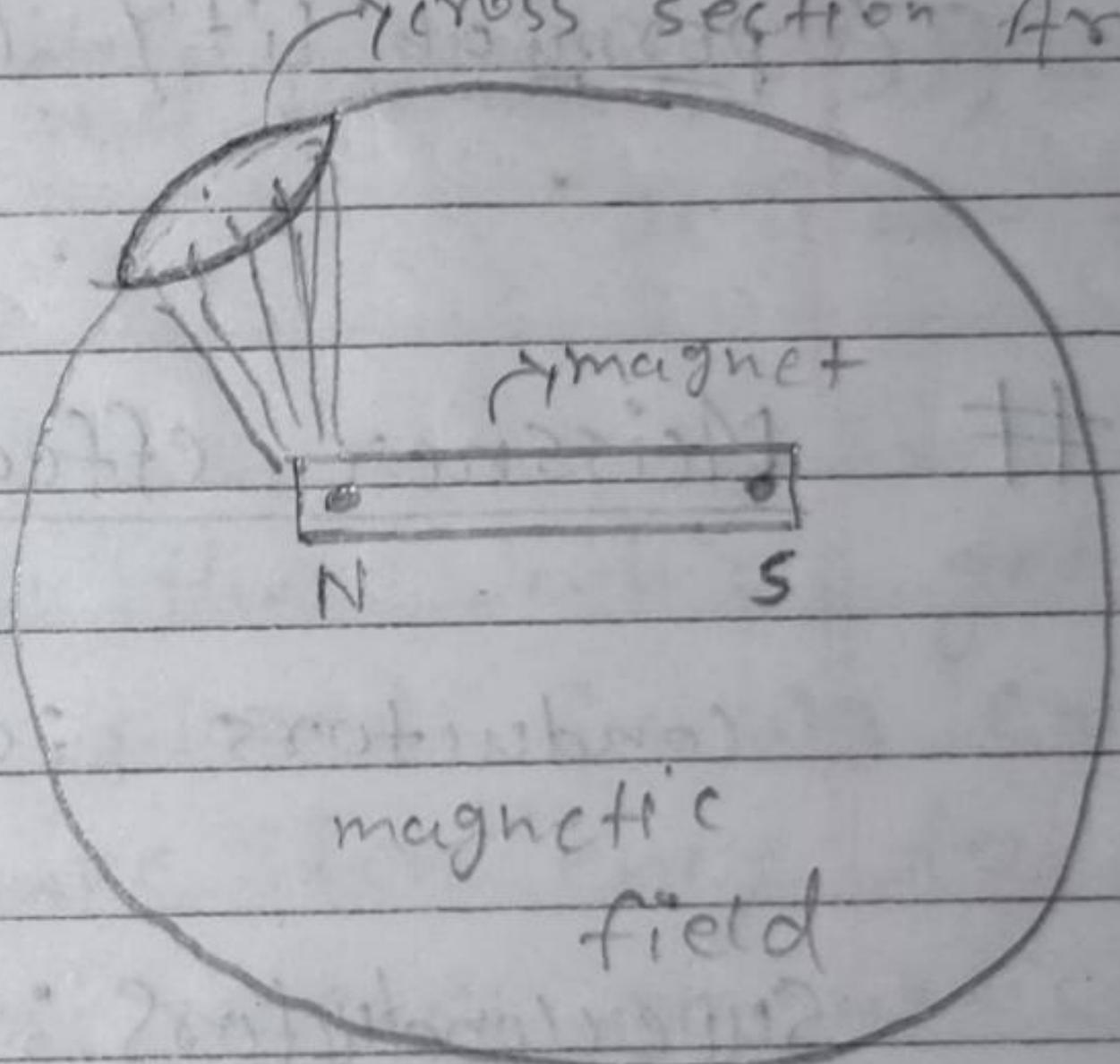

quantity:- scalar quantity

$$1 \text{ Wb} = 10^8 \text{ max}$$

$$\therefore \phi = BA \quad \left\{ \text{when } \theta = 90^\circ \right\}$$

$$\Rightarrow B = \frac{\phi}{A}$$

$$\Rightarrow B = \frac{\text{Wb}}{\text{m}^2}$$

$$\Rightarrow B = \text{Tesla} = \text{N/A.m}$$

Dimensional formula :-

$$\phi = M L^2 T^{-2} A^{-1}$$

$$B = M L^0 T^{-2} A^{-1}$$

Ans.2. Electromagnetic Induction:-

Whenever the relative motion b/w magnet and coil the linked magnetic flux of the coil is changed causes of this electromotive force is induced this phenomena is called the Electromagnetic Induction. If the Galvanometer is connected or circuit is closed then flowing current is called induced current.

Ans.3. There is 2 law's of Faraday's law of electromagnetic induction :-

(i)

Electromagnetic current is produced until the magnet comes in rest.

It means whenever magnet is more near the coil then the induced current is produced in the coil.

(ii)

induced current is directly proportional to the rate of change of magnetic flux (ϕ_m) + self inductance

$$\Rightarrow -\mathbf{E} \propto \frac{d\phi}{dt}$$

where $\phi \rightarrow$ magnetic flux.
 $I \rightarrow$ induced current.

$$\Rightarrow \mathbf{E} = -\frac{d\phi}{dt}$$

Q.4 Define Lenz law for electromagnetic induction?

Q.5 What do you understand by self induction and self inductance?

Q.6 Derive an expression for self inductance for a solenoid.

Fleming Right Hand Rule :-

According to the Fleming right hand rule, if we stretch our fore finger, middle finger and thumb such that they are mutually perpendicular to each other then thumb shows 'motion of the conductor', fore finger shows 'magnetic field' then middle finger shows 'direction of induced current'.


Ans.4 Lenz law :- According to Lenz law, the direction of induced current is such that it always opposes the change which produces it.

This Lenz law is similar to conservation of energy.

Lenz law :- The direction of induced current is such that it opposes the change or the cause which produces each.

(or)

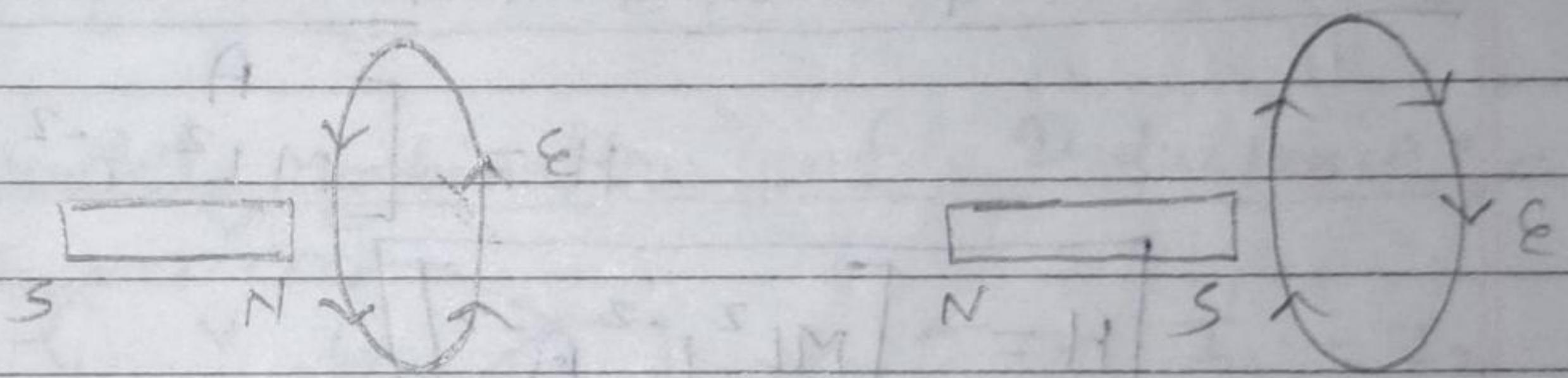Lenz law :- If we take north pole of magnet near the coil then direction of induced current is Anti clockwise And when we take south pole of a magnet near the coil then direction of induced current is clock wise,



Aus' 5. Self induction :- The when the electric current passes through any coil the and change the flow of current then linked magnetic flux of the coil is changed this phenomena is known as self induction.

$$\phi \propto I$$

$$\phi = LI \quad \text{where } L \rightarrow \text{self inductance}$$

$$L = \frac{\phi}{I}$$

self inductance

(or) inductance.

SI unit of L :-

$$L = \frac{\phi}{I}$$

$$L = \frac{Wb}{Ampere}$$

$$L = \text{Henry} (H)$$

Henry :- The ratio of weber and Ampere is known as Henry.


Dimensional formula :- $H = \frac{ML^2 T^{-2} A^{-1}}{A}$

$$H = \left[ML^2 T^{-2} A^{-2} \right]$$

$$H = \boxed{\left[ML^2 T^{-2} A^{-2} \right]}$$

→ solenoid.

Ans. 6.

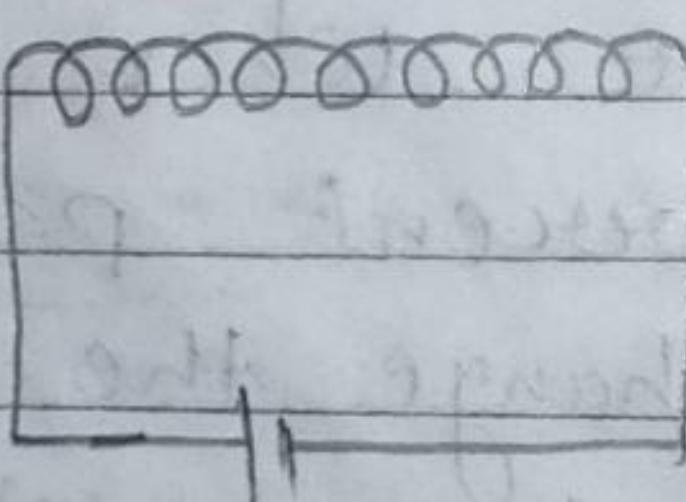

$$\Rightarrow L = \frac{\phi}{I}$$

$$\therefore B = \mu_0 N I$$

$$\Rightarrow L = \frac{\mu_0 N I A}{I} \quad \{ \text{for solenoid} \}$$

$$\Rightarrow L = \frac{\mu_0 N I A}{I}$$

$$\Rightarrow L = \mu_0 N A$$

$$\therefore N = n l$$

$$\Rightarrow L = \mu_0 n (n l) A$$

$$\Rightarrow L = \boxed{\mu_0 n^2 l A}$$

$$\therefore n = \frac{N}{l}$$

$$\Rightarrow L = \mu_0 \frac{N^2}{l^2} l A$$

$$\Rightarrow L = \boxed{\frac{\mu_0 N^2 A}{l}}$$


$$\# \Rightarrow \phi \propto I$$

$$\Rightarrow \phi = LI$$

$$\Rightarrow e = -\frac{d\phi}{dt} \Rightarrow \boxed{e = -L \frac{dI}{dt}}$$

Date _____
Page _____

Series combination of Inductance :-

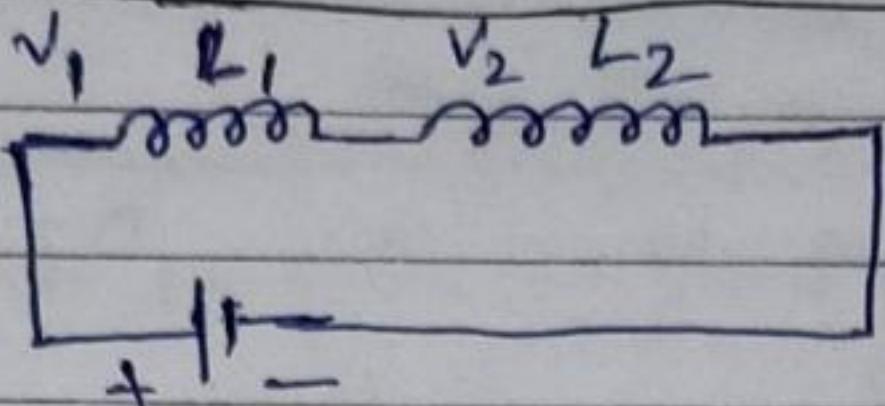

$$V = e = -L \frac{dI}{dt}$$


$$\because V = V_1 + V_2$$

$$\Rightarrow -L \frac{dI}{dt} = -L_1 \frac{dI}{dt} + \left(-L_2 \frac{dI}{dt} \right)$$

$$\Rightarrow -L \frac{dI}{dt} = -\frac{dI}{dt} (L_1 + L_2)$$

$$\Rightarrow \boxed{L = L_1 + L_2} \quad \text{where } L \rightarrow \text{inductance.}$$

Parallel combination of Inductance :-

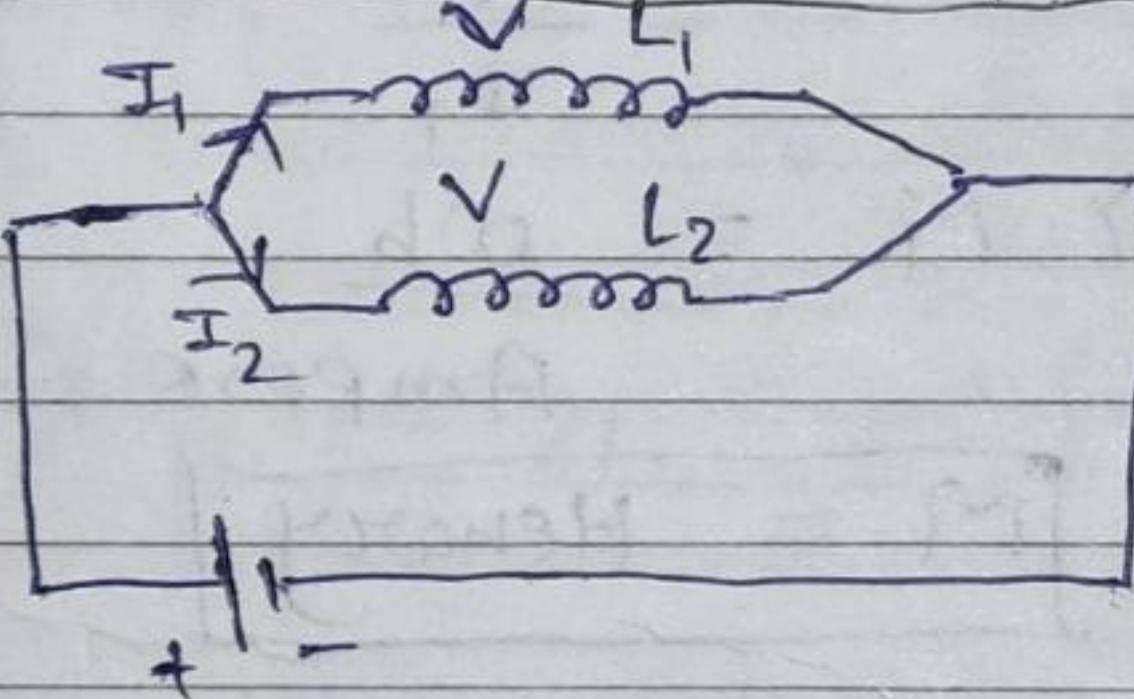

$$I = I_1 + I_2$$

$$\therefore V = e = -L \frac{dI}{dt}$$

$$\Rightarrow \frac{dI}{dt} = -\frac{e}{L}$$

$$\Rightarrow I = \int -\frac{e}{L} dt$$

$$\Rightarrow I = -\frac{e}{L} \int dt$$

$$\Rightarrow \boxed{I = -\frac{et}{L}}$$

Now,

$$\Rightarrow I = I_1 + I_2$$

$$\Rightarrow \frac{-et}{L} = -\frac{et}{L_1} + \left(-\frac{et}{L_2} \right)$$


$$\Rightarrow \frac{-et}{L} = -et \left(\frac{1}{L_1} + \frac{1}{L_2} \right)$$

$$\Rightarrow \boxed{\frac{1}{L} = \frac{1}{L_1} + \frac{1}{L_2}}$$

where,
 $L \rightarrow$ inductance.

Q.7. What is mutual induction? and induction and mutual inductance?

Ans: \rightarrow

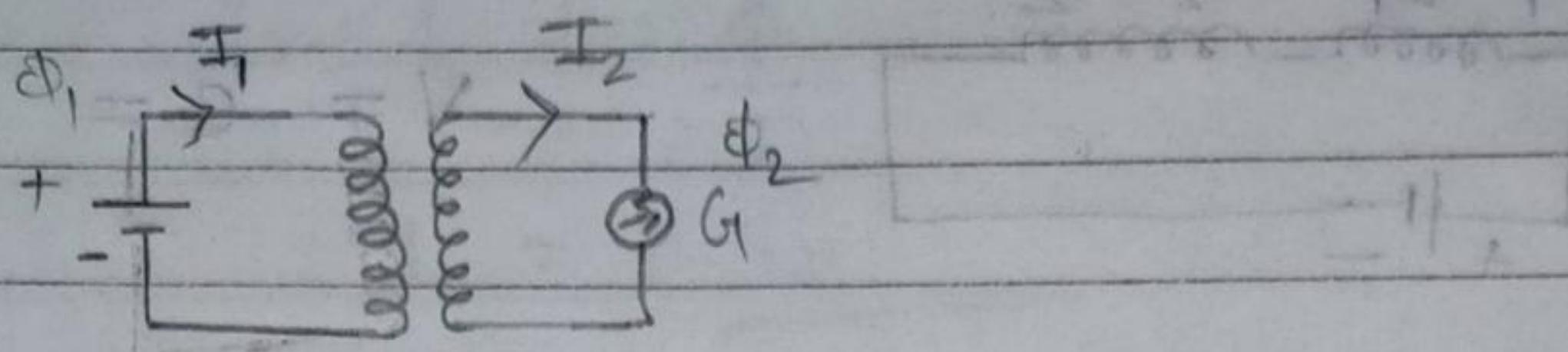

$$\phi_2 \propto I_1$$

$\phi_2 = M I_1$ where $M \rightarrow$ mutual inductance.

$$M = \frac{\phi_2}{I_1}$$


Unit of M :-

$$\Rightarrow M = \frac{\phi_2}{I_1}$$

$$\Rightarrow M = \frac{Wb}{Ampere}$$

$$\Rightarrow [M = \text{Henry}]$$

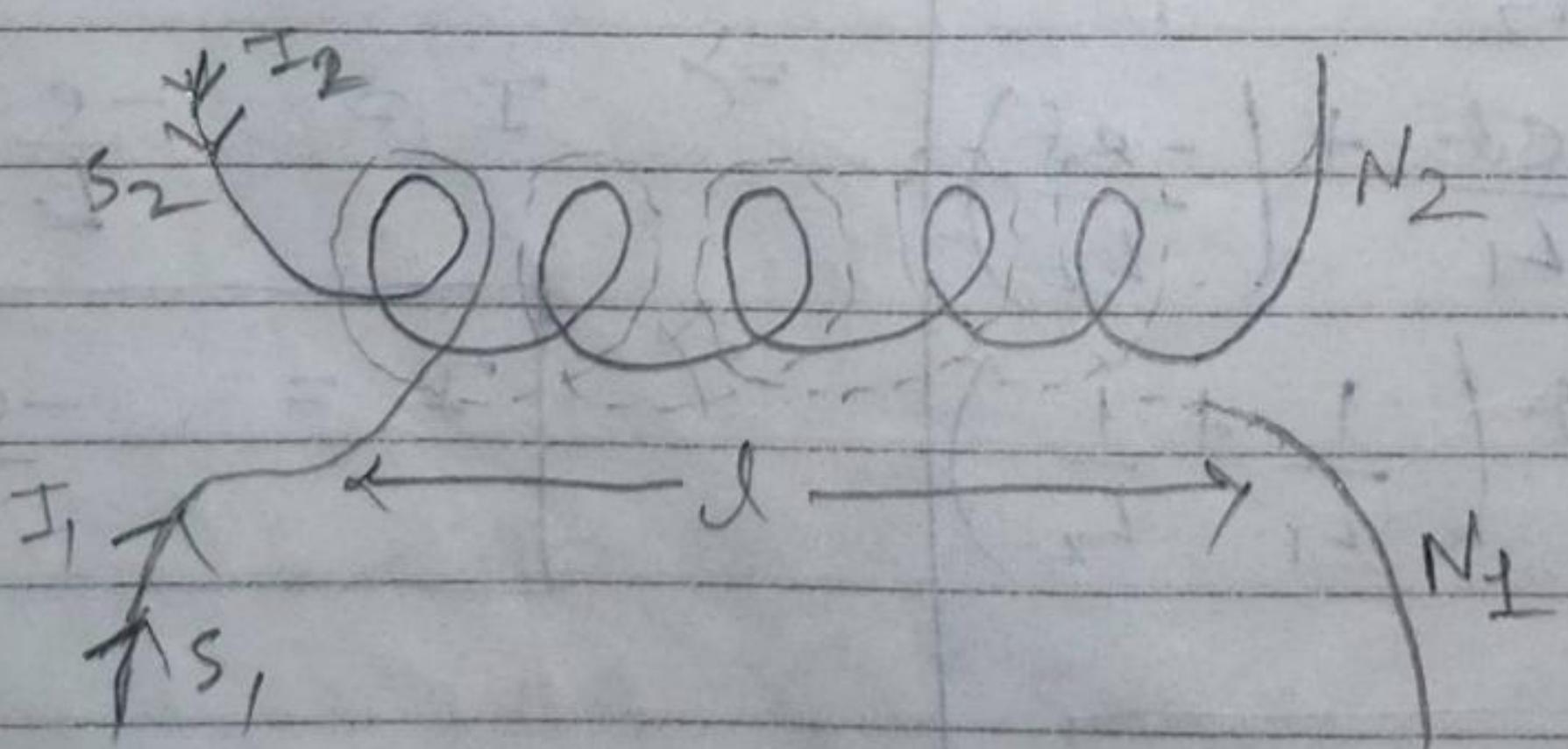Mutual inductance for current carrying solenoids:-



$$\therefore N = nl$$

$$\Rightarrow M_{12} = \frac{\phi_2}{I_1} = \frac{B A}{I_1} = \frac{\mu_0 n_1 I_1 A}{I_1} = \frac{\mu_0 n_1 A}{I_1}$$

$$= \frac{N_2 (\mu_0 n_1 A) A}{I_1}$$

$$\begin{aligned}
 &= \mu_0 N_2 n_1 A \\
 &= \mu_0 n_2 l n_1 A \quad [\because N_2 = n_2 l] \\
 &= \mu_0 n_1 n_2 A l \\
 \Rightarrow M_{12} &= \frac{\mu_0 N_1 N_2 A}{l}
 \end{aligned}$$

$$\begin{aligned}
 M_{21} &= \frac{\phi_1}{I_2} \\
 &= \frac{\mu_0 B_2 \pi}{I_2} \\
 &= \frac{N_1 \mu_0 n_2 I_2 A}{I_2} \\
 &= \mu_0 N_1 n_2 A
 \end{aligned}$$

$$M_{21} = \frac{\mu_0 N_1 n_2 A}{l}$$

$$M_{12} = M_{21} = M$$

Q.8. What do you mean by motional electromotive force and find out their formula?

Q.9 What is eddy current? write it's application.


Aus. 9. \rightarrow Eddy current is induced current.

\rightarrow Eddy current is also called "foucault current."

Sudden change of rate of relative motion in magnet and coil then induced current is called eddy current.

Application :- It is used for emergency break in train.

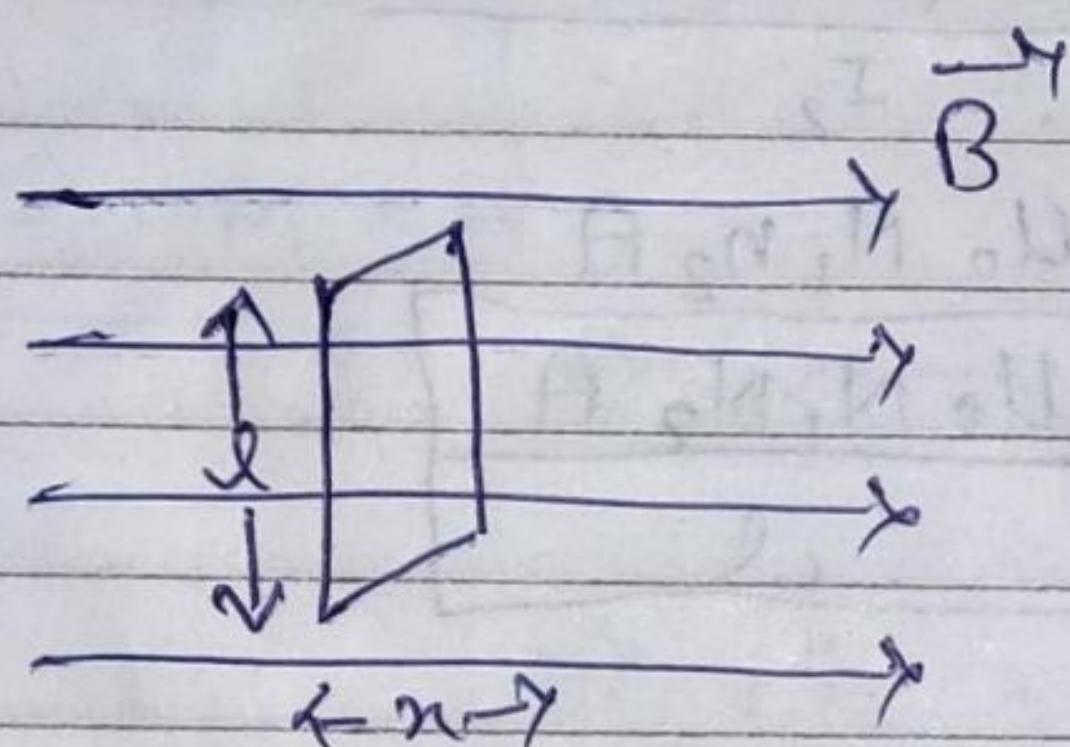Ans.8. The electromotive force due to motion is called motional electromotive force.



$$\Rightarrow e = \frac{d\phi}{dt}$$

$$\Rightarrow e = \frac{d(BA)}{dt}$$

$$\Rightarrow e = B \frac{dA}{dt}$$

$$\Rightarrow e = B \frac{d(l \times w)}{dt}$$

$$\Rightarrow e = Bd \frac{dn}{dt}$$

$$\Rightarrow e = Blv$$
 where, $e \rightarrow$ electromotive force.
 $v \rightarrow$ velocity
 $l \rightarrow$ length of coil
 $B \rightarrow$ magnetic field.


Q.10 What is dynamo (A.C. generator)? Explain its principle.

Q.11 With the help of graph define Alternating current.

Ans. to Q.10 A dynamo is a device which converts the mechanical energy into electrical energy, this device is known as the Dynamo.

Dynamo is work on the Electromagnetic Induction

$\rightarrow \omega$ (Angular velocity)

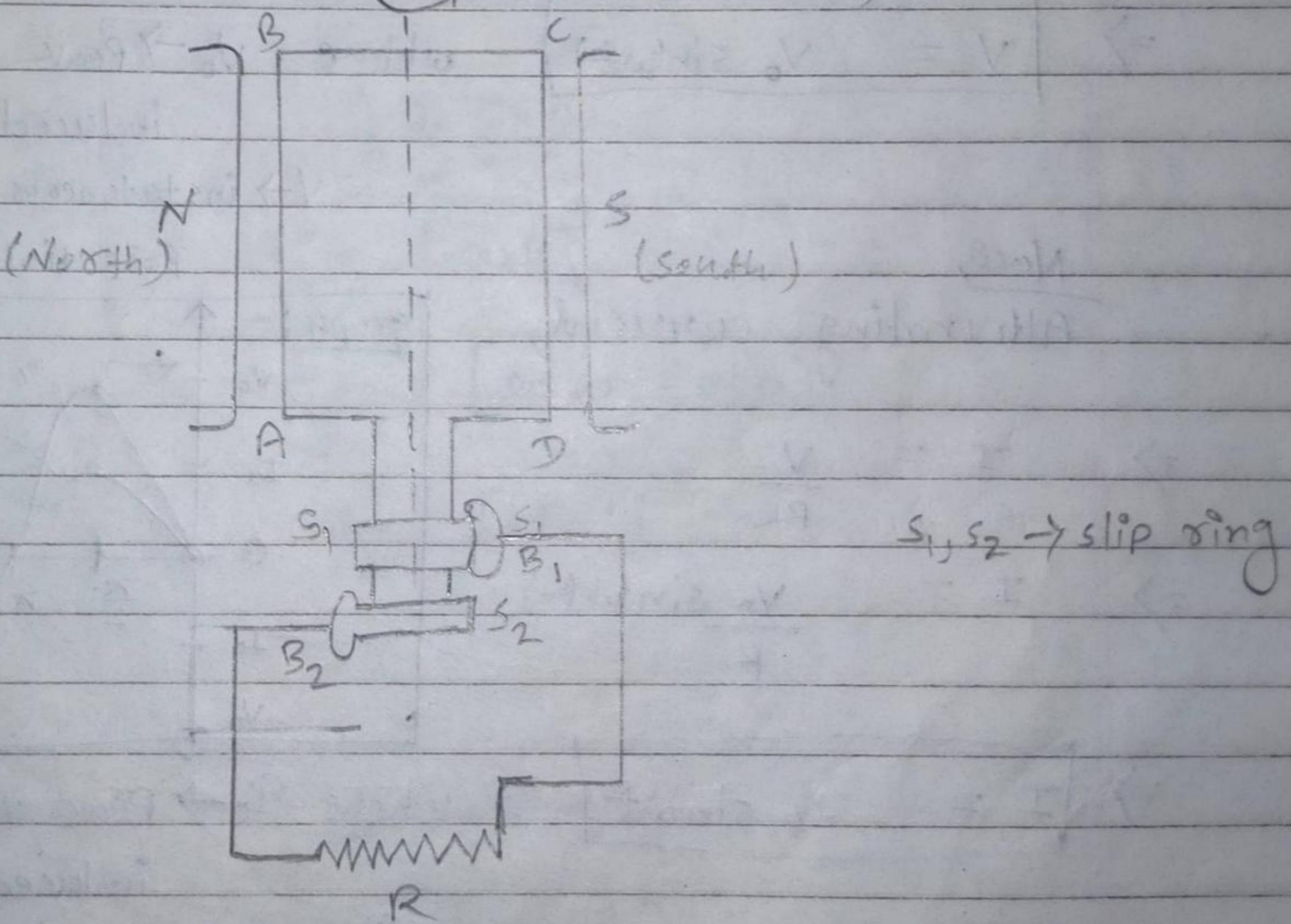

$$\therefore \omega = \frac{\theta}{t}$$

$$\boxed{\theta = \omega t}$$

$$\Rightarrow V = e = -\frac{d\phi}{dt}$$

$$\Rightarrow V = e = -\frac{d}{dt} (NBA \cos \theta) \quad \left\{ \begin{array}{l} \because \phi = BA \cos \theta \\ \text{for no. of terms,} \\ \phi = NBA \cos \theta \end{array} \right.$$

where, $N \rightarrow$ no. of terms.

$$\Rightarrow V = e = -NBA \frac{d}{dt} \cos(\omega t) \quad [\because \theta = \omega t]$$

$$\Rightarrow V = e = -NBA (-\sin \omega t) \omega$$

$$\Rightarrow V = e = NBA \omega \sin \omega t$$

$$\Rightarrow \boxed{V = V_0 \sin(\omega t)} \quad \text{where } V_0 \rightarrow \text{Peak Value of induced E.m.f.}$$

$V \rightarrow$ instantaneous E.m.f or


NoC,

Alternating current,

$$\Rightarrow I = \frac{V}{R}$$

$$\Rightarrow I = \frac{V_0 \sin(\omega t)}{R}$$
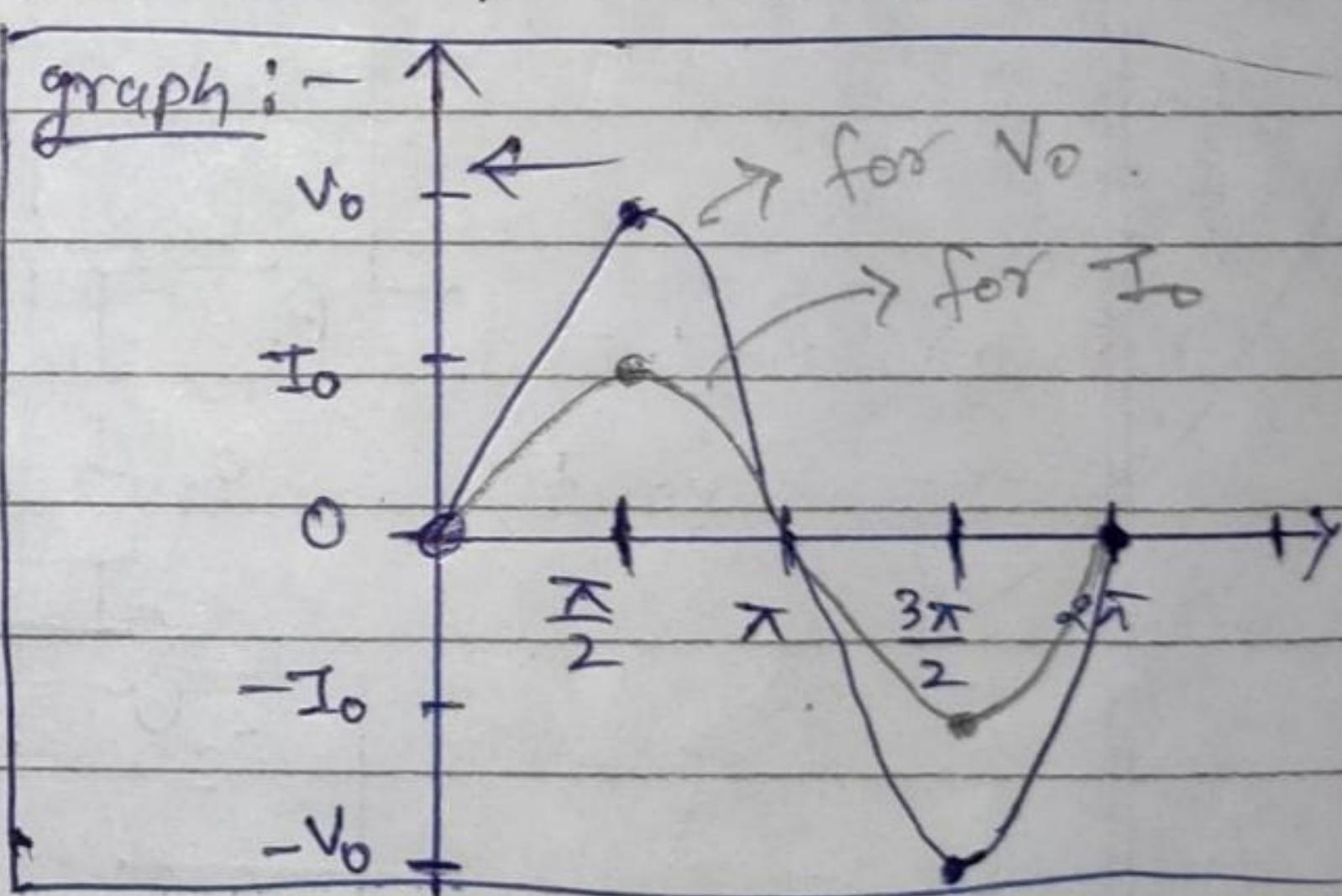
$$\Rightarrow \boxed{I = I_0 \sin \omega t}$$



Where $I_0 \rightarrow$ Peak value of induced current.

$I \rightarrow$ Instantaneous current.

$\omega t = 0$	0°	90°	180°	360°	270°
V	0	V_0	V_0	0	$-V_0$
I	0	I_0	I_0	0	$-I_0$

Q.12 prove that the average value of Alternating current (A.C) in one cycle is zero.

Q.13. Find the average value of A.C current in half cycle.

Q.14 Why A.C. does not show magnetic effect and chemical effect also?

Q.15. Derive the formula for root mean square value of A.C.

Q.16. A.C. is more dangerous than D.C. why?


Alternating current :- The magnitude and direction is continuous change this current is known as Alternating current.

$$\begin{aligned} \text{Ans.12. } I_{\text{average}} &= \int_0^{2\pi} \frac{I_0 \sin \theta}{2\pi} \\ &= -\frac{I_0}{2\pi} [\cos \theta]_0^{2\pi} \\ &= -\frac{I_0}{2\pi} [\cos 2\pi - \cos 0] \\ &= -\frac{I_0}{2\pi} [1 - 1] \\ &= 0 \end{aligned}$$

$$\begin{aligned} \text{Ans.13 } I_{\text{average}} &= \int_0^{\pi} \frac{I_0 \sin \theta}{\pi} \\ &= \frac{I_0}{\pi} [-\cos \theta]_0^{\pi} \\ &= -\frac{I_0}{\pi} [\cos \pi - \cos 0^\circ] \\ &= -\frac{I_0}{\pi} [-1 - 1] \end{aligned}$$

$$I_{\text{average}} = \frac{2I_0}{\pi}$$

Ans. 15. graph of A.C. :-

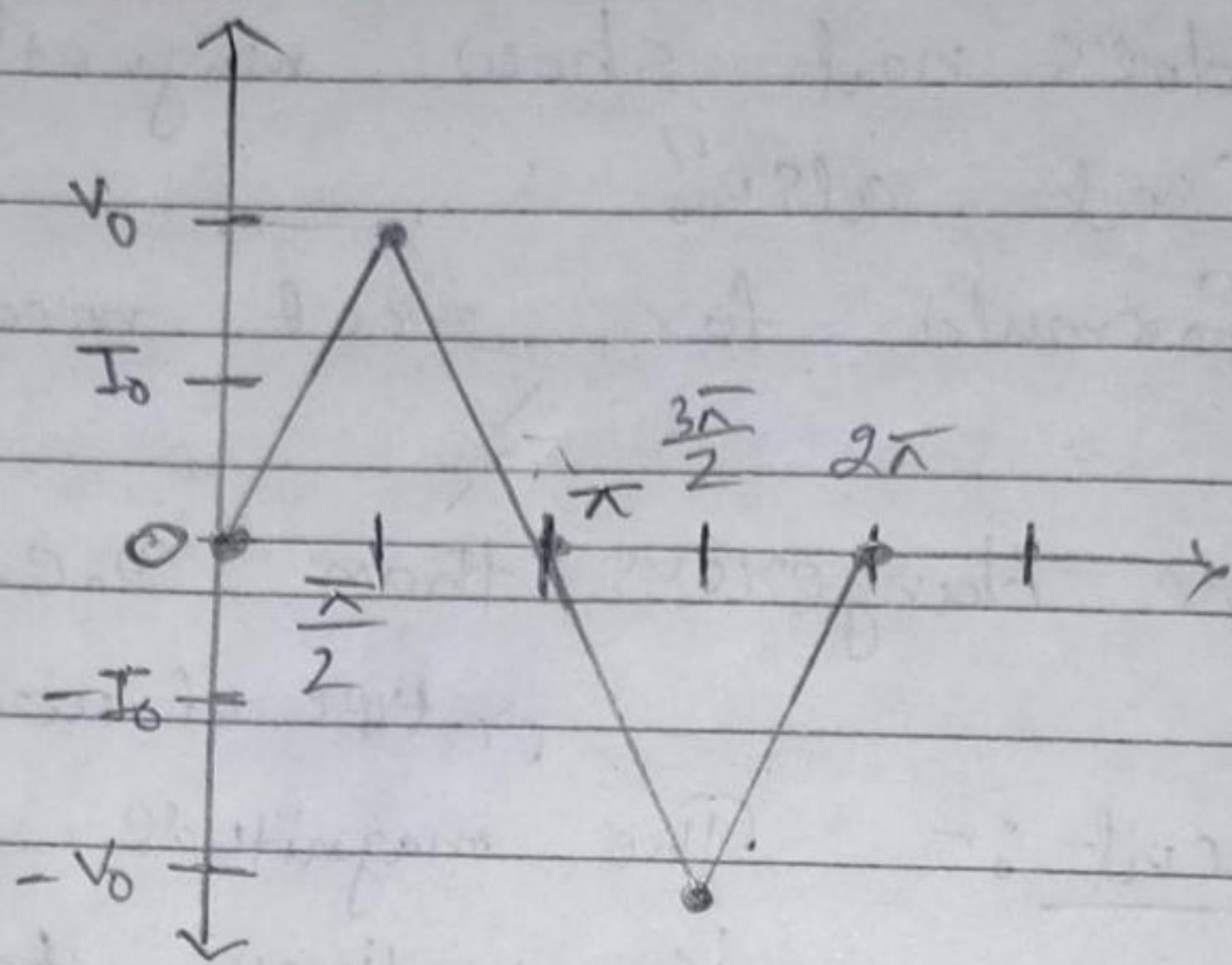

Magnetic effect for A.C. :-

in graph of A.C., the positive part \rightarrow represent North pole and negative part \rightarrow represent South pole so at position of 2π (complete 1 cycle) ~~post~~ magnetic effect is zero because positive and negative part cancel each other.

Chemical effect for A.C. :-

in graph of A.C., positive part represent forward reaction and negative part represent backward reaction, when it complete one cycle mean in position of 2π the positive and negative part cancel each other hence also chemical effect is zero.

Aus. 15

$$\text{Root mean square value} = \sqrt{\frac{\int (I_0 \sin \omega t)^2 d\theta}{2\pi}}$$

$$= \sqrt{\frac{I_0^2}{2\pi} \int (\sin^2 \omega t) d\theta}$$

$$= \sqrt{\frac{I_0^2}{2\pi} \int \sin^2 \theta d\theta}$$

$$= I_0 \sqrt{\frac{1}{2\pi} \int \sin^2 \theta d\theta}$$

$$\therefore \cos 2\theta = 1 - 2\sin^2 \theta$$

$$\Rightarrow -2\sin^2 \theta = \cos 2\theta - 1$$

$$\Rightarrow 2\sin^2 \theta = 1 - \cos 2\theta$$

$$\Rightarrow \sin^2 \theta = \frac{1 - \cos 2\theta}{2}$$

$$\begin{aligned}\text{R.m.s. Value} &= I_0 \sqrt{\frac{1}{2\pi} \int_0^{2\pi} \frac{1 - \cos 2\theta}{2} d\theta} \\&= I_0 \sqrt{\frac{1}{4\pi} \int_0^{2\pi} (1 - \cos 2\theta) d\theta} \\&= I_0 \sqrt{\frac{1}{4\pi} \left[\int_0^{2\pi} 1 d\theta - \int_0^{2\pi} \cos 2\theta d\theta \right]} \\&= I_0 \sqrt{\frac{1}{4\pi} \left[(0)_0^{2\pi} - \left(\frac{\sin 2\theta}{2} \right)_0^{2\pi} \right]}\end{aligned}$$

$$\text{R.M.S Value} = I_0 \sqrt{\left[\left(\frac{\theta}{4\pi} \right)_0^{2\pi} - \left(\frac{\sin 2\theta}{8\pi} \right)_0^{2\pi} \right]}$$

$$= I_0 \sqrt{\frac{2\pi}{4\pi} - \frac{\sin 2(2\pi)}{8\pi}}$$

$$= I_0 \sqrt{\frac{1}{2} - \frac{0}{8\pi}}$$

$$= I_0 \sqrt{\frac{1}{2}}$$

$$\text{R.M.S. value} = \frac{I_0}{\sqrt{2}}$$

Q. 17 Define Reactance & Impedance.

Q. 18 what is the effect on A.C. when a resistance is containing in A.C. source?

Q. 19. what is the effect on A.C. when a capacitance is containing in A.C. source?

Q. 20 what is the effect on A.C. when a inductance is containing in A.C. source?

Ans. 17. Reactance & Impedance is the type of resistance with S.I unit ohm (Ω).

representation :-

Reactance \rightarrow (X)

Impedance \rightarrow (Z)


X Reactance :- The resistance due to capacitance and Inductance is called Reactance.

X Impedance :- The resistance due to ~~the two~~ or three ~~parameters~~ factors (Resistance, Capacitance, Inductance) that resistance is called Impedance.

Ans. 18 In A.C. there is no effect by the resistance.

D.C. is affected by the resistance.

Ans. 19

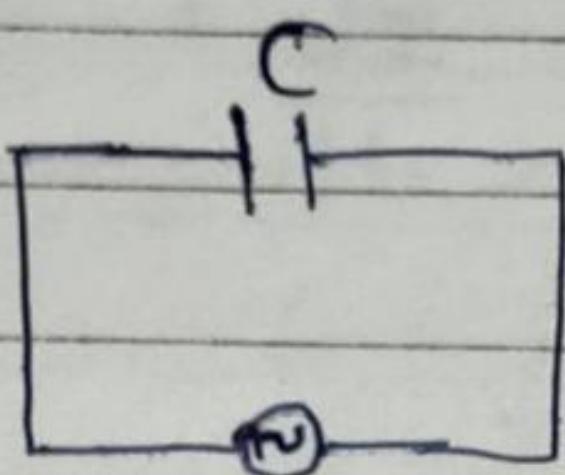

$$\Rightarrow V = V_0 \sin \omega t$$

$$\therefore I = \frac{dQ}{dt}$$

$$= \frac{d(CV)}{dt}$$

$$= C \frac{dV}{dt}$$

$$= C V_0 \frac{d(\sin \omega t)}{dt}$$

$$= C V_0 \frac{\omega \sin \omega t}{dt}$$

$$= C V_0 (\omega \sin \omega t)$$

$$= \omega C V_0 \cos \omega t$$

$$= I_0 \cos \omega t$$

$$\Rightarrow \boxed{I = I_0 \sin(\omega t + \frac{\pi}{2})}$$

In A.C. when we connect ^{capacitor} ~~capacitance~~ then the current is ^{increasing by} ~~leading~~ $\frac{\pi}{2}$ phase diff.

$$\Rightarrow I = I_0 \sin(\omega t + \frac{\pi}{2})$$

where, $I_0 = \omega C V_0$


$$\Rightarrow \frac{I_0}{V_0} = \omega C$$

$$\Rightarrow \frac{V_0}{I_0} = \frac{1}{\omega C}$$

$$\Rightarrow \frac{V_0}{I_0} = \frac{1}{\omega C} = X_C$$

$$\Rightarrow X_C = \frac{1}{\omega C} \quad (\text{Capacitive reactance.})$$

graph :-

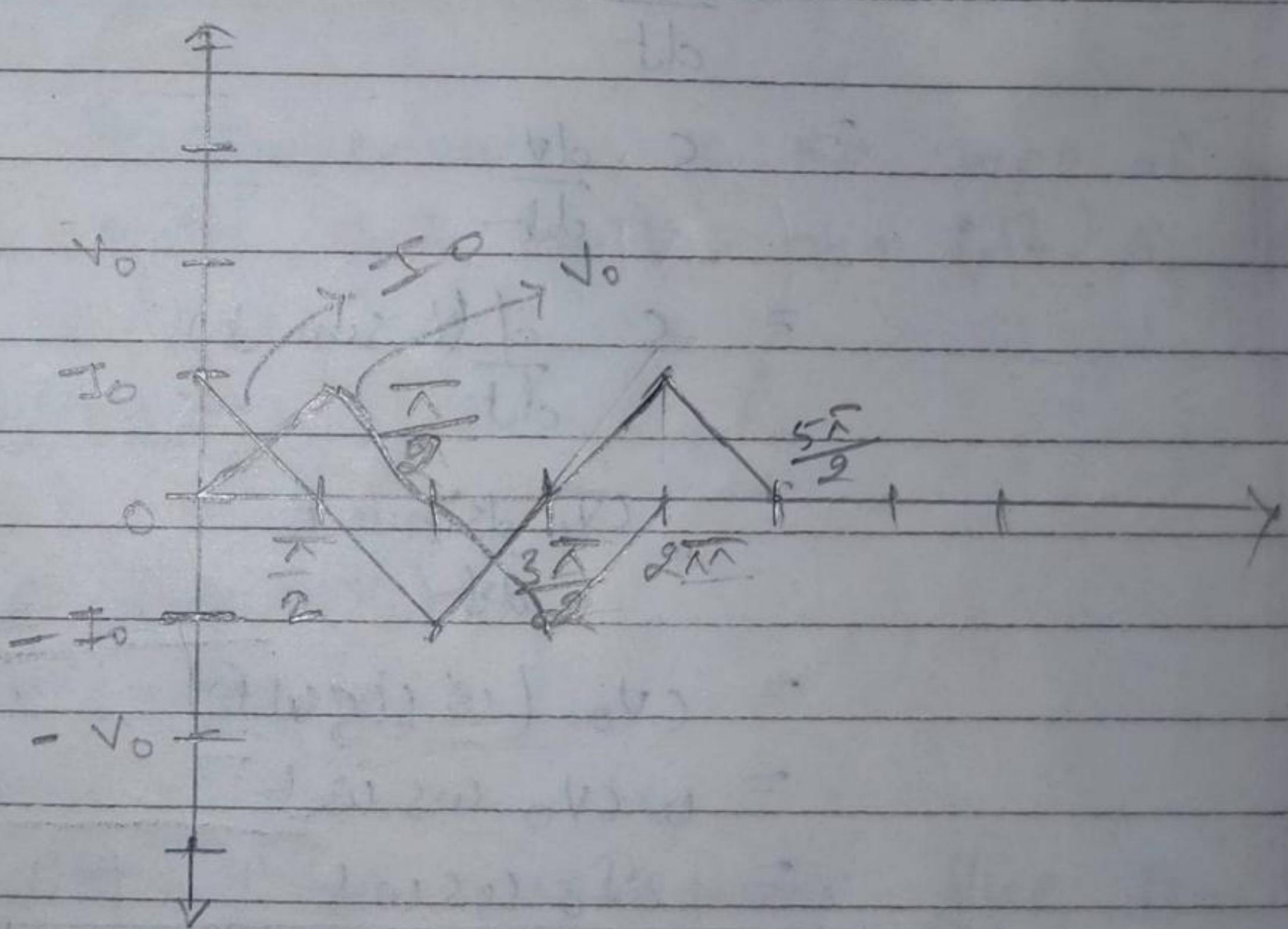

Aus. 20) $\therefore V = e = L \frac{dI}{dt}$

$$\therefore I = I_0 \sin \omega t$$

$$\Rightarrow V = L \frac{dI}{dt}$$

$$\Rightarrow V = L \frac{d}{dt} I_0 \sin \omega t$$

$$\Rightarrow V = L I_0 \cancel{\sin} (\cos \omega t) \omega$$

$$\Rightarrow V = \omega L I_0 \cos \omega t$$

$$\Rightarrow V = \omega L I_0 \sin (\omega t + 90^\circ)$$

$$\Rightarrow V = V_0 \sin (\omega t + 90^\circ)$$

In A.C. source when we connect inductor the potential diff. is leading by $\frac{\pi}{2}$ phase diff.

$$\therefore V = \frac{dLI}{dt}$$

$$\Rightarrow \int V_0 \sin \omega t \, dt = LI$$

$$\Rightarrow V_0 \left[-\frac{\cos \omega t}{\omega} \right] = LI$$

$$\Rightarrow -\frac{V_0}{\omega L} \cos \omega t = I$$

$$\Rightarrow I = -I_0 \sin \left(\omega t + \frac{\pi}{2} \right)$$

$$\Rightarrow I = \overset{(os)}{I_0} \sin \left(\frac{3\pi}{2} - \omega t \right)$$

$$\Rightarrow -\frac{V_0}{\omega L} \cos \omega t = I$$

$$\Rightarrow I = -I_0 \cos \omega t$$

$$\Rightarrow I = I_0 \sin(\omega t - 90^\circ)$$

$$\Rightarrow I = I_0 \sin(\omega t - 90^\circ)$$

Q.21 Why D.C. does not flow through the capacitor but easily flows through the inductor why?

Ans.

$$\text{Capacitive Reactance } (X_C) = \frac{1}{\omega C}$$

(frequency) is zero in D.C.

$$X_C = \frac{1}{(0) C}$$

$$X_C = \frac{1}{0}$$

$$X_C = \infty$$

Resistance is infinity ~~in capacit~~ ^{D.C.} through the conductor while D.C., therefore current can not easily flow.

$$\Rightarrow \text{Inductive Reactance } (X_L) = \omega L \\ = 0 L \\ = 0$$

Resistance = 0.

Resistance is zero then inductance therefore current can ~~not~~ flow easily through inductance while current is D.C.


Q.22 What is L-R circuit? Derive the expression for impedance, maximum current and phase diff.

Q.23 What is C-R circuit? Derive the expression for the impedance, maximum current and phase diff.

Q.24 What is L-C circuit? Derive the expression for the impedance, maximum current and phase diff.

Q.25 What is L-C-R circuit? Derive the expression for impedance, maximum current and phase diff.


Ans.22.

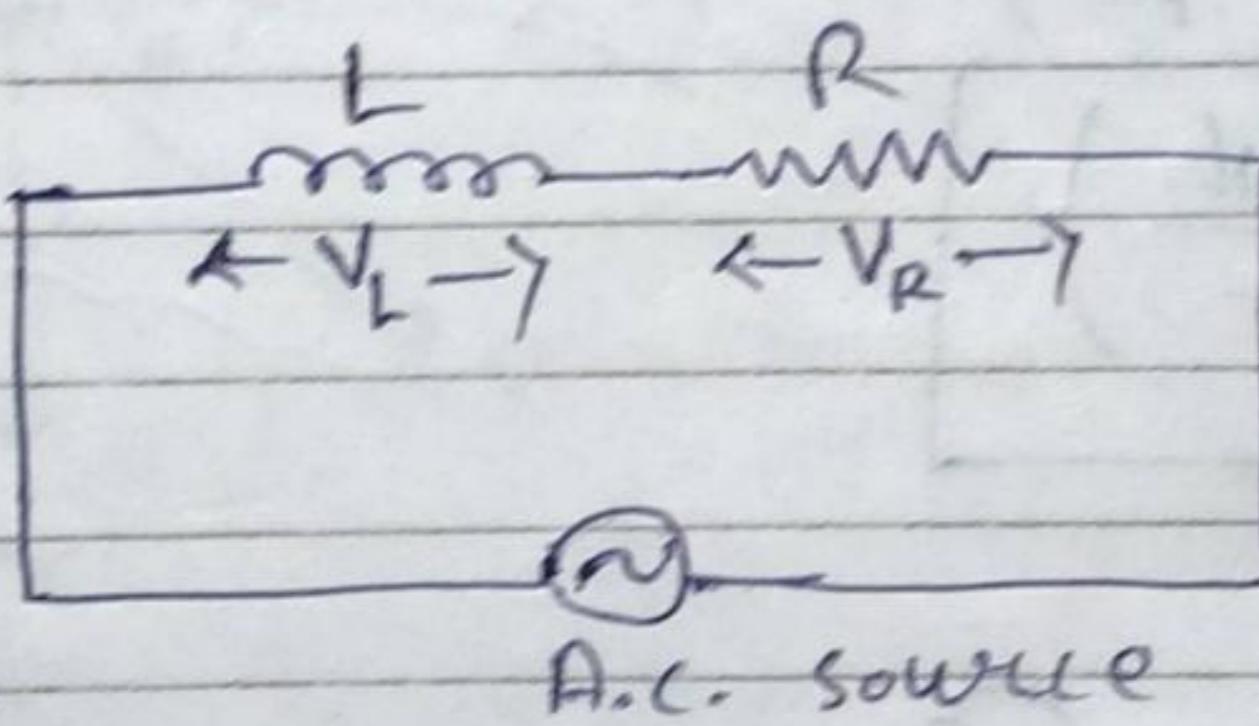

$$V_R = IR$$

$$V_L = IX_L$$

$$V_C = IX_C$$

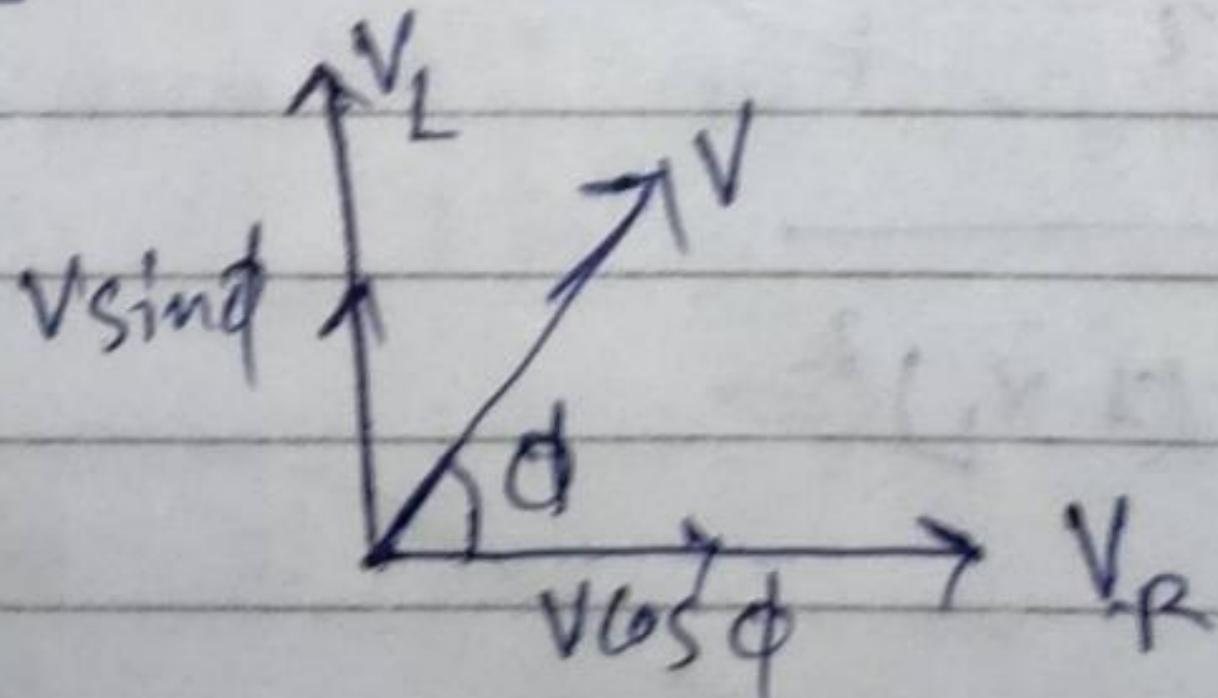

$$V_L = V \sin \phi \rightarrow \textcircled{i}$$

$$V_R = V \cos \phi \rightarrow \textcircled{ii}$$

Dividing \textcircled{i} / \textcircled{ii}

$$\Rightarrow \frac{V_L}{V_R} = \frac{V \sin \phi}{V \cos \phi}$$

$$\Rightarrow \frac{V_L}{V_R} = \tan \phi$$

$$\Rightarrow \tan \phi = \frac{V_L}{V_R}$$

$$\Rightarrow \phi = \tan^{-1} \left(\frac{I R}{I L} \right)$$

$$\Rightarrow \phi = \tan^{-1} \left(\frac{X_L}{R} \right)$$

$$\Rightarrow \boxed{\phi = \tan^{-1} \left(\frac{\omega L}{R} \right)}$$

Squaring and Adding \textcircled{i} and \textcircled{ii},

$$\Rightarrow V^2 + V_R^2 = V^2$$

$$\Rightarrow V = \sqrt{V_L^2 + V_R^2}$$

$$\Rightarrow V = \sqrt{(IR)^2 + (IX_L)^2}$$

$$\Rightarrow \frac{V}{I} = \sqrt{R^2 + X_L^2}$$

$$\Rightarrow Z = \sqrt{R^2 + X_L^2}$$

Impedance

and


$$\Rightarrow \boxed{\text{Impedance } (Z) = \sqrt{R^2 + X_L^2}}$$

and,


$$\text{current } (I_o) = \frac{V_o}{R} = \frac{V_o}{Z}$$

$$\boxed{I_o = \frac{V_o}{\sqrt{R^2 + X_L^2}}}$$

Ans-23)

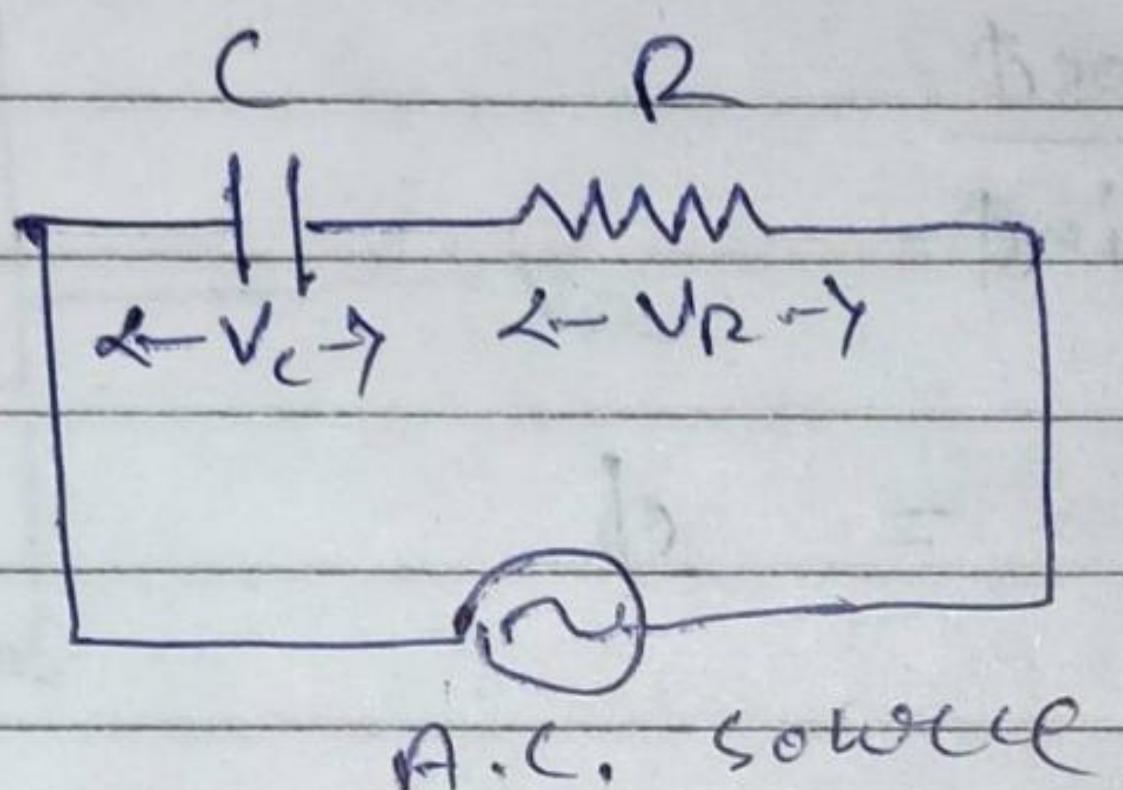

A.C. source.

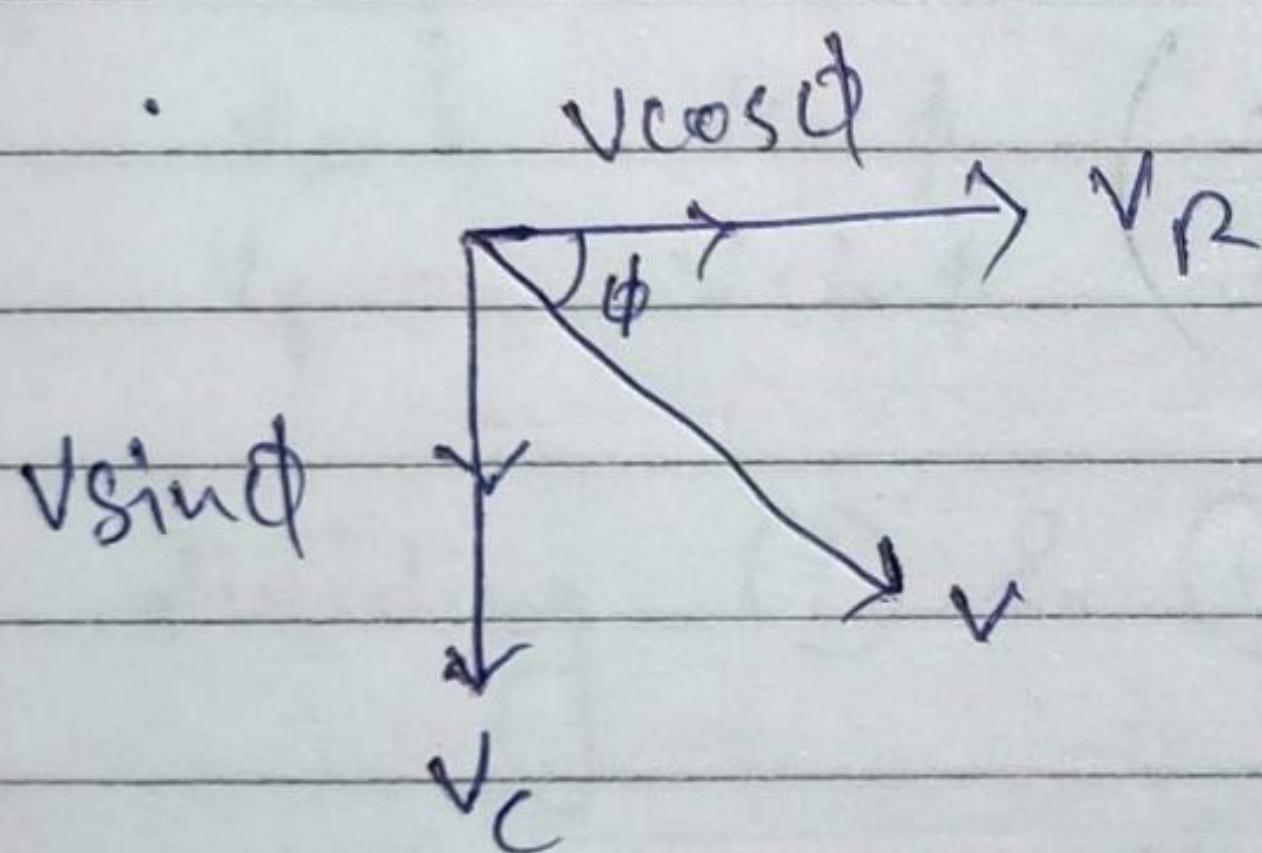

$$V_R = I R$$

$$V_C = I X_C$$

$$V_L = I X_L$$

$$V_R = V \cos \theta$$

$$V_C = V \sin \theta$$

→ → ①
→ ②

Squaring and adding eqn ① & ②

$$\Rightarrow V_R^2 + V_C^2 = V^2$$

$$\Rightarrow V = \sqrt{(IR)^2 + (Ix_c)^2}$$

$$\Rightarrow \frac{V}{I} = \sqrt{R^2 + x_c^2}$$

$$\Rightarrow \boxed{Z = \sqrt{R^2 + x_c^2}}$$

dividing ① & ②,

$$\Rightarrow \frac{v_R}{v_c} = \frac{v \cos \phi}{v \sin \phi}$$

$$\Rightarrow \tan^{-1} \left(\frac{v_c}{v_R} \right) = \phi$$

$$\Rightarrow \phi = \tan^{-1} \left(\frac{Ix_c}{IR} \right)$$


$$\Rightarrow \boxed{\phi = \tan^{-1} \left(\frac{x_c}{R} \right)}$$

$$\therefore I = \frac{V}{R}$$

$$I = \frac{V}{Z}$$

$$\boxed{I = \frac{V}{\sqrt{R^2 + x_c^2}}}$$

Ans. 25.

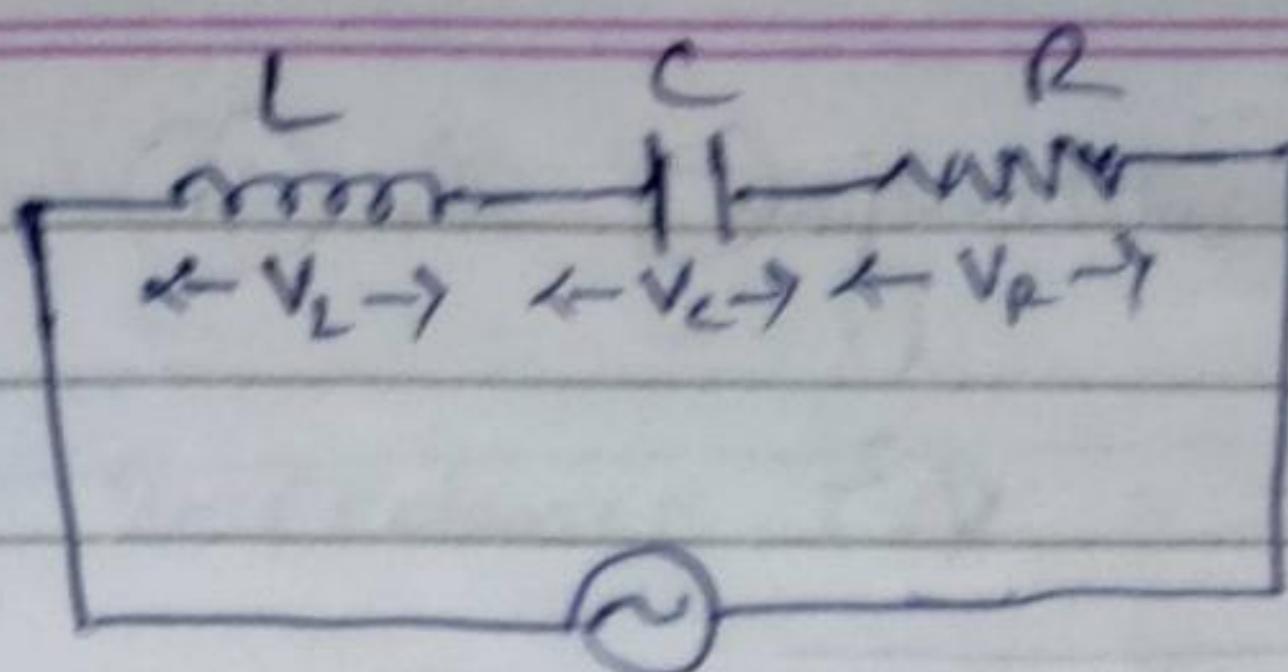



A.C. source.

$$V_R = IR$$

$$V_C = IX_C$$

$$V_L = IX_L$$

$$V_I = V_L - V_C$$

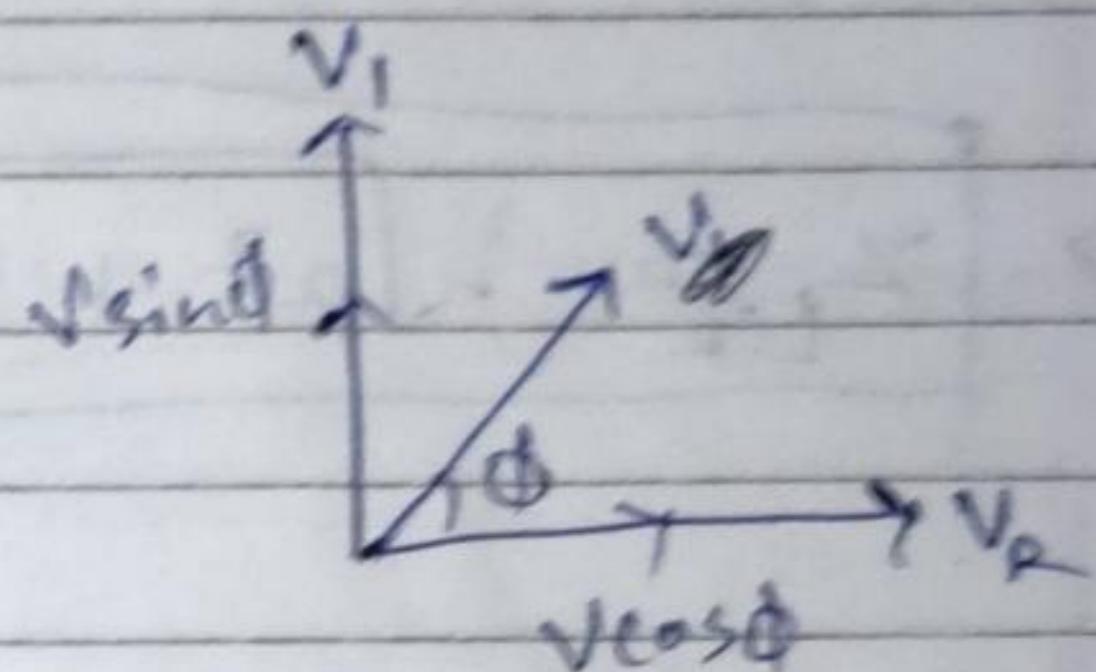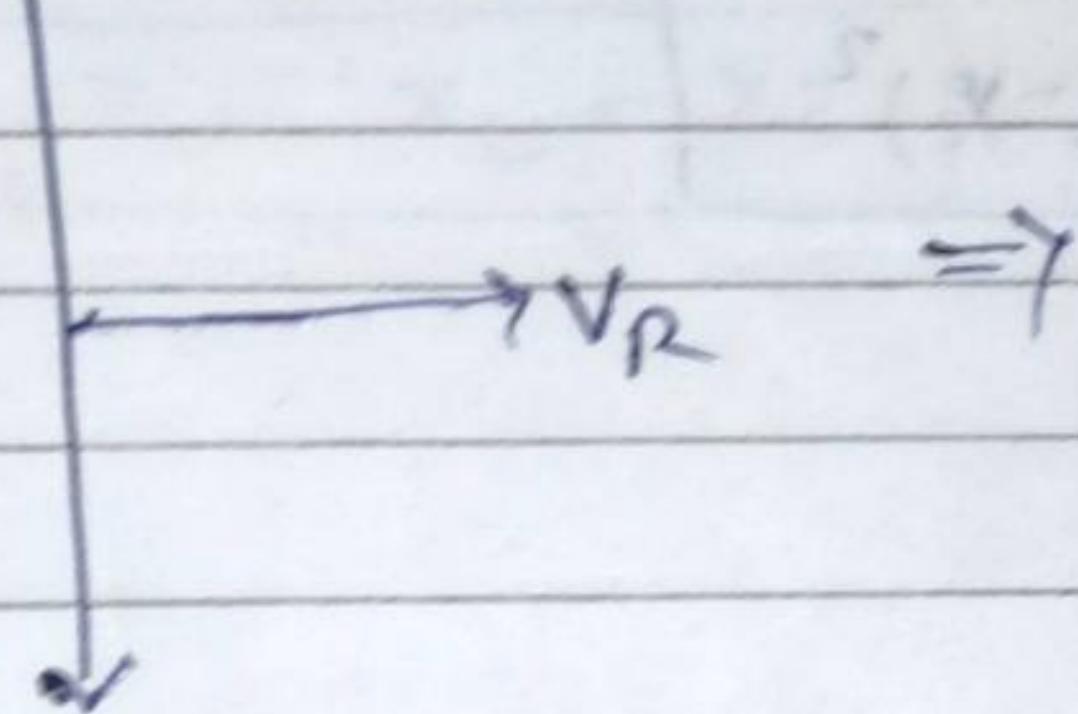

$$\Rightarrow V_R = V \cos \phi \rightarrow \textcircled{1}$$

$$\Rightarrow V_I = V \sin \phi \rightarrow \textcircled{2}$$

dividing \textcircled{1} & \textcircled{2},

$$\Rightarrow \frac{V_R}{V_I} = \frac{V \cos \phi}{V \sin \phi}$$

$$\Rightarrow \phi = \tan^{-1} \left(\frac{V_I}{V_R} \right)$$

$$\Rightarrow \phi = \tan^{-1} \left(\frac{V_L - V_C}{V_R} \right)$$

$$\phi = \tan^{-1} \left(\frac{IX_L - IX_C}{IR} \right)$$

$$\boxed{\phi = \tan^{-1} \left(\frac{X_L - X_C}{R} \right)}$$

Squaring and adding i & ii

$$\Rightarrow V_1^2 + V_R^2 = V^2$$

$$\Rightarrow V = \sqrt{V_R^2 + V_1^2}$$

$$\Rightarrow V = \sqrt{(IR)^2 + (X_L - X_C)^2}$$

$$\Rightarrow \frac{V}{I} = \sqrt{R^2 + (X_L - X_C)^2}$$


$$\Rightarrow Z_{LCR} = \sqrt{R^2 + (X_L - X_C)^2}$$

$$\therefore I = \frac{V_0}{Z}$$

$$I = \frac{V_0}{\sqrt{R^2 + (X_L - X_C)^2}}$$

Ans.


Ans. 24)

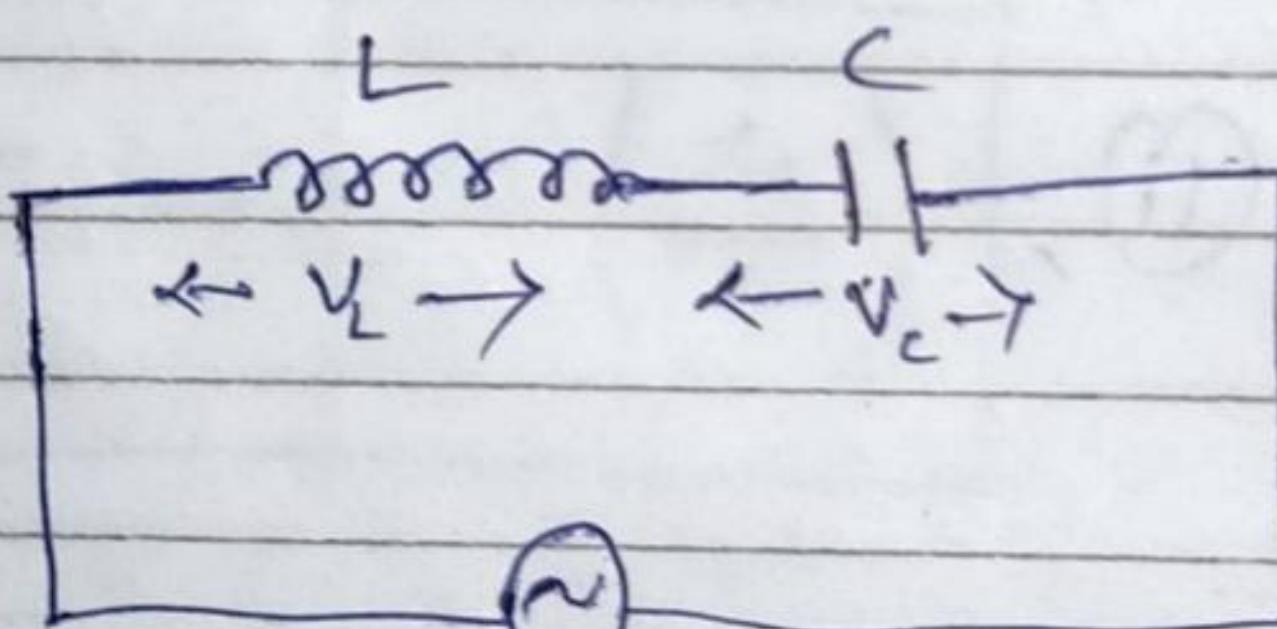

$$V_R = IR$$

$$V_L = IX_L$$

$$V_C = IX_C$$

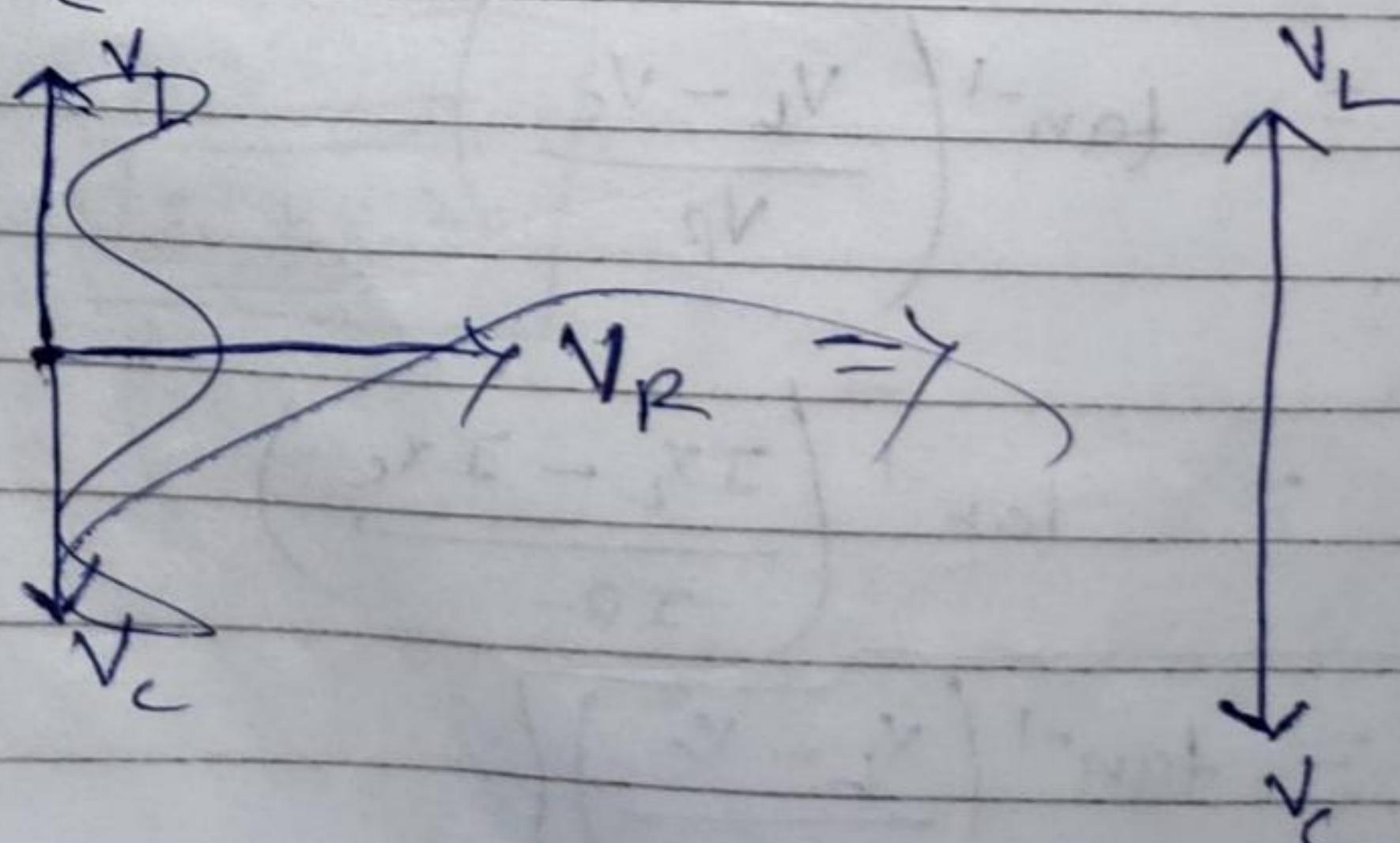

$$\Rightarrow V_p = V_L - V_C$$

$$\Rightarrow \sqrt{R} = Ix_L - Ix_C$$

$$\Rightarrow \frac{\sqrt{R}}{I} = x_L - x_C$$

$$\Rightarrow \boxed{Z = x_L - x_C} \quad \underline{\text{Ans.}} \quad (\text{Impedance})$$

Q.26 what is Resonance circuit, Resonance current, Resonance frequency, Condition for Resonance.

Q.27 Derive the formula for resonance frequency.

Q.28 write the principle of choke coil and derive the formula for power D.C. Dissipate.

Ans.26. Resonance current:- The maximum current flowing in L.C.R circuit is called Resonance current.

Condition for Resonance:-

$$\Rightarrow [X_L - X_C = 0]$$

Resonance frequency:-

$$\Rightarrow X_L - X_C = 0$$

$$\Rightarrow X_L = X_C$$

$$\Rightarrow \omega L = \frac{1}{\omega C}$$

$$\Rightarrow \omega^2 = \frac{1}{LC}$$

$$\Rightarrow \omega = \frac{1}{\sqrt{LC}}$$

$$\therefore \omega = \frac{2\pi}{T} = \frac{2\pi}{T} = 2\pi f$$

$$\therefore \omega = 2\pi\nu$$

$$\Rightarrow \omega = \frac{1}{\sqrt{LC}}$$

$$\Rightarrow 2\pi\nu = \frac{1}{\sqrt{LC}}$$

$$\Rightarrow \nu = \frac{1}{2\pi\sqrt{LC}}$$

This is called resonance frequency.

Resonance circuit :- In L.C.R circuit, the phase difference b/w

voltage (V) and current (I) is zero or constant.
this circuit is called Resonance circuit.

Principle of

Ans.28 choke coil :- A pure inductor is used to control the alternating current.



formula for power dissipate :-

$$\Rightarrow P = VI$$

$$= V_0 \sin \omega t I_0 \sin (\omega t - \frac{\pi}{2})$$

$$= \frac{V_0 I_0}{2} 2 \sin \omega t \sin (\omega t - \frac{\pi}{2})$$

$$= \frac{V_0 I_0}{2} \left[\cos \left\{ \omega t - \left(\omega t - \frac{\pi}{2} \right) \right\} - \cos \left(\omega t + \omega t - \frac{\pi}{2} \right) \right]$$

$\because 2 \sin A \sin B = [\cos(A-B) - \cos(A+B)]$ is called potential represented by "V", S.I

$$= \frac{V_0 I_0}{2} \left[\cos \frac{\pi}{2} - \cos(2\omega t - \frac{\pi}{2}) \right]$$

$$= \frac{V_0}{\sqrt{2}} \cdot \frac{I_0}{\sqrt{2}} \left[\cos \frac{\pi}{2} - \cos(2\omega t - \frac{\pi}{2}) \right]$$

$$= V_{\text{r.m.s.}} I_{\text{r.m.s.}} \left[\cos \frac{\pi}{2} - \cos(2\omega t - \frac{\pi}{2}) \right]$$

$$= V_{\text{r.m.s.}} I_{\text{r.m.s.}} \left[\cos \frac{\pi}{2} - \cos(\omega t + \omega t - \frac{\pi}{2}) \right]$$

$$= V_{\text{r.m.s.}} I_{\text{r.m.s.}} \left[\cos \frac{\pi}{2} - \cos(2\omega t - \frac{\pi}{2}) \right]$$

$$= V_{\text{r.m.s.}} I_{\text{r.m.s.}} \left[\cos \frac{\pi}{2} \oplus \cos \left(\frac{\pi}{2} - 2\omega t \right) \right]$$

$$\left[\because \cos(-\theta) = \cos(\theta) \right]$$

Average of $\cos(\frac{\pi}{2} - 2\omega t)$ is zero when completed full cycle.

$$P = V_{\text{r.m.s.}} I_{\text{r.m.s.}} \left(\cos \frac{\pi}{2} \right)$$

$$P = V_{\text{r.m.s.}} I_{\text{r.m.s.}} (0)$$

$$P = 0$$

There is no power dissipate in which pure inductor is used.

$$\therefore \omega = \frac{\Theta}{t}$$